

CMPE 110 Lab 1 Part 1: First-Order Passive RC Circuits

Leonardo Blas

Abstract—The purpose of this lab project is to learn about resistance, capacitance, the time constant, and rise and fall times in RC circuits with a pulse generator.

I. INTRODUCTION

This lab project is based on the implementation of 4 pairs of RC circuits in LTspice, where all pairs have the same time constant ($\tau = 1 \mu s$) but different R and C values. Each pair of circuits is composed of almost identical RC series circuits, where the only difference is that the positions of the resistor and capacitor are swapped—see **Figure 3** and **Figure 5**.

We are asked to:

- Using the resistor values, $R = 1K\Omega$, $10K\Omega$, $100K\Omega$ and $1M\Omega$, **calculate** the capacitor values for a time constant value of $\tau = 1 \mu s$ for each resistor.
- Use each RC combination from part (a) in the circuits below and measure the rise time and the fall time at the output, v_{out} . You need to connect a pulse generator that changes between 0 and 5V at the input of the circuit and observe the circuit response at the output terminal using the oscilloscope. Note that the rise time is measured from 20% of the output voltage to 80% of the output voltage. Similarly, the fall time is measured from 80% of the output voltage to 20% of the output voltage.
- Use each RC combination from part (a) in the circuits below and find the time constant. Use the mathematical expressions of v_{out} for each circuit to extract the time constant, and then use the measured time and voltage values from your oscilloscope to determine the time constant.

Figure 1. Instructions.

And to produce the following results:

Show the calculated and measured rise and fall times and time constants in an Excel table and explain the error between the measured and calculated values. In cases where you cannot take sensible measurements, show the results on your scope screen in the report and explain why measurements could not be made.

Figure 2. Expected results.

Before assembling the 4 pairs of RC circuits, the capacitance values that would make each pair of circuits' τ equal to 1 are calculated. For this, we use the RC circuits' equation:

- $\tau = RC$

And determined that:

R	L	$R * C$
$1K\Omega$	$1nF$	$1\mu s$
$10K\Omega$	$100pF$	$1\mu s$
$100K\Omega$	$10\mu F$	$1\mu s$
$1M\Omega$	$1pF$	$1\mu s$

Table 1. R and C values for the 4 pairs of circuits.

After setting up each circuit, measurements of the rise and fall times are made, and then used to obtain a new τ . For this we use the RL circuits' equations:

- $V_{out} = V_s \left(1 - e^{-\frac{t}{RC}} \right)$, for charging capacitors.
- $V_{out} = V_s \left(e^{-\frac{t}{RC}} \right)$, for discharging capacitors.

Finally, the theoretical and measured values for the time constant and the rise and fall times are compared, for each individual circuit.

A. Parts List

- 0-5V pulse generator. See **Figure 4** and **Figure 6**.
- $1K\Omega$, $10K\Omega$, $100K\Omega$, and $1M\Omega$ resistors
- $1nF$, $1pF$, $10pF$, and $100pF$ capacitors
- Grounding components
- LTspice software

II. DESCRIPTION OF THE CIRCUITS' SCHEMATICS

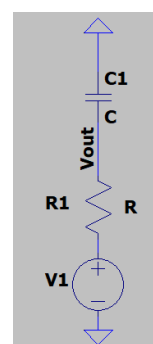


Figure 3. Configuration 1.

Vinitial[V]:	0
Von[V]:	5
Tdelay[s]:	0
Trise[s]:	1u
Tfall[s]:	1u
Ton[s]:	1m
Tperiod[s]:	2m
Ncycles:	2

Figure 4. The pulse generator’s settings for configuration 1 circuits.

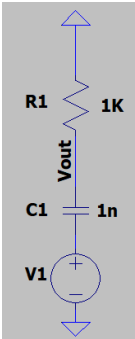


Figure 5. Configuration 2.

Vinitial[V]:	0
Von[V]:	5
Tdelay[s]:	0
Trise[s]:	1n
Tfall[s]:	1n
Ton[s]:	1m
Tperiod[s]:	2m
Ncycles:	2

Figure 6. The pulse generator’s settings for configuration 2 circuits.

III. WAVEFORMS AND RESULTS

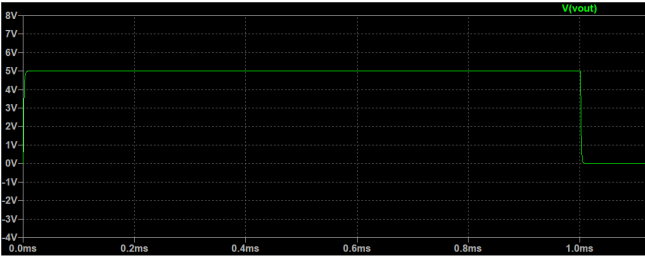


Figure 7. General waveform for configuration 1 circuits.

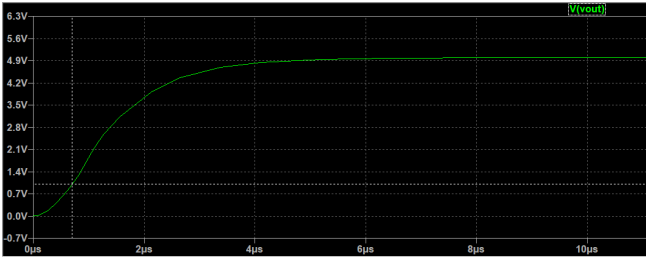


Figure 8. General rise zoom-in for configuration 1 circuits.

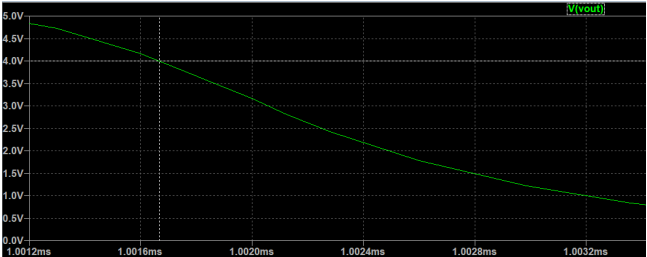


Figure 9. General fall zoom-in for configuration 1 circuits.

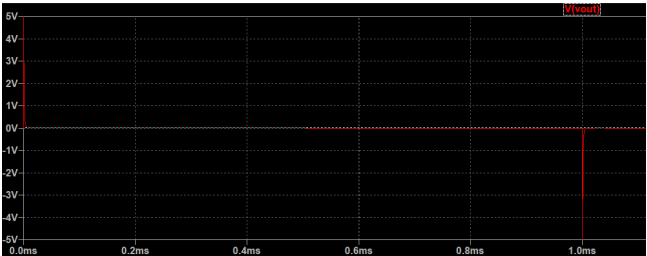


Figure 10. General waveform for configuration 2 circuits.

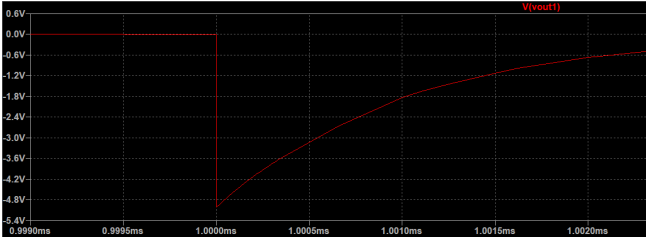


Figure 11. General rise zoom-in for configuration 2 circuits.

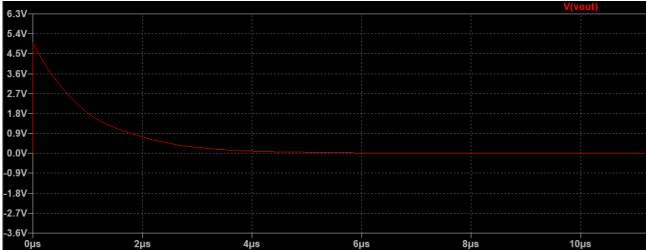


Figure 12. General fall zoom-in for configuration 2 circuits.

Rise time data				
R	Configuration 1 circuits' times (μs)		Configuration 2 circuits' times (μs)	
1K Ω	t1: 0.70509873	t2: 2.2392538	t1: 1000.2299	xt2: 1001.6082
10K Ω	t1: 0.70509873	t2: 2.2392538	t1: 1000.2299	t2: 1001.6082
100K Ω	t1: 0.70509873	t2: 2.2392538	t1: 1000.2299	t2: 1001.6082
1M Ω	t1: 0.70509873	t2: 2.2392538	t1: 1000.2299	t2: 1001.6082

Table 2. Rise time data table.

Fall time data				
R	Configuration 1 circuits' times (μs)		Configuration 2 circuits' times (μs)	
1K Ω	t1: 1001.6993	t2: 1003.1944	t1: 0.22844656	t2: 1.6613897
10K Ω	t1: 1001.6993	t2: 1003.1944	t1: 0.22844656	t2: 1.6625634
100K Ω	t1: 1001.6993	t2: 1003.1944	t1: 0.22844656	t2: 1.6648702
1M Ω	t1: 1001.6993	t2: 1003.1944	t1: 0.22844656	t2: 1.6648702

Table 3. Fall time data table.

Rise times calculations table (t2-t1)		
R	Configuration 1 circuits' rise time (μs)	Configuration 2 circuits' rise time (μs)
1K Ω	1.53415507	1.3783
10K Ω	1.53415507	1.3783
100K Ω	1.53415507	1.3783
1M Ω	1.53415507	1.3783

Table 4. Rise times calculations table

Fall times calculations table (t2-t1)		
R	Configuration 1 circuits' fall time (μs)	Configuration 2 circuits' fall time (μs)
1K Ω	1.4951	1.43294314
10K Ω	1.4951	1.43411684
100K Ω	1.4951	1.43642364
1M Ω	1.4951	1.43642364

Table 5. Fall times calculations table

Type	$V_{out}(V)$	$t_{exp}(\mu s)$	$\tau_{calc}(\mu s)$	% error
Rise	-1	1.3783	0.8564	14.34%
	-1	1.3783	0.8564	14.34%
	-1	1.3783	0.8564	14.34%
	-1	1.3783	0.8564	14.34%
	4	1.53415507	0.9532	4.68%
	4	1.53415507	0.9532	4.68%
	4	1.53415507	0.9532	4.68%
	4	1.53415507	0.9532	4.68%
Fall	1	1.43294314	0.8903	10.97%
	1	1.43411684	0.8911	10.89%
	1	1.43642364	0.8925	10.75%
	1	1.43642364	0.8925	10.75%
	1	1.4951	0.9289	7.11%
	1	1.4951	0.9289	7.11%
	1	1.4951	0.9289	7.11%
	1	1.4951	0.9289	7.11%

Table 6. τ calculated using theoretical V_{out} and experimental t values.

Type	$V_{out}(V)$	$\tau_{calc}(\mu s)$	$t_{calc}(\mu s)$	% error
Rise	-1	0.8564	1.37832263	0.0016%
	-1	0.8564	1.37832263	0.0016%
	-1	0.8564	1.37832263	0.0016%
	-1	0.8564	1.37832263	0.0016%
	4	0.9532	1.53411622	0.0025%
	4	0.9532	1.53411622	0.0025%
	4	0.9532	1.53411622	0.0025%
	4	0.9532	1.53411622	0.0025%
Fall	1	0.8903	1.43288257	0.0042%
	1	0.8911	1.43417012	0.0037%
	1	0.8925	1.43642333	$2.1 \times 10^{-5}\%$
	1	0.8925	1.43642333	$2.1 \times 10^{-5}\%$
	1	0.9289	1.49500687	0.0062%
	1	0.9289	1.49500687	0.0062%
	1	0.9289	1.49500687	0.0062%
	1	0.9289	1.49500687	0.0062%

Table 7. t calculated using theoretical V_{out} and calculated τ values.

IV. DISCUSSION

This lab project's recorded measurements fall along the lines of the theoretical values for our 8 circuits, as demonstrated through the relatively low percent error results, nevertheless there are still some discrepancies between the calculated and theoretical values for some quantities, particularly the time constant. Such errors could be explained through the accuracy of our equipment—selecting desired voltage levels was particularly challenging in our oscilloscope—but moreover, by the fact that an “adequate” measurement of one time constant is performed at 63 and 37% of the output voltage, rather than 80 and 20%. This claim is supported by the accuracy of our time measurements. Our time measurements reached certain

time constants without much friction—see **Table 7**—but could not be used to obtain $\tau = 1$.

V. DESCRIPTION OF THE LEARNING EXPERIENCE

This lab project was a challenge that pushed me to learn in-depth details related to RC circuits. This was an incentive and an opportunity to not only use the existing knowledge I acquired from our lectures and our textbook, but also research, learn, and verify my current knowledge on RC circuits. To further and to supplement my education on RC circuits, I visited several higher education institution's websites, which provided me with additional resources on waveforms and how to approach them using different methods, to acquire the different possible variables of interest.

VI. CONCLUSION

In conclusion, this lab experiment was a fruitful RC circuits learning experience, where we tried to obtain a $\tau = 1$ from V_{out} at 80 and 20%, rather than 63 and 37%. We had to inquire and look for further educational resources to explain our relatively large percent error values—see **Table 6**—until we ultimately acknowledged a possible cause for these margins. Finally, while researching and trying to understand possible error sources, we became more familiar with RC circuits in the process.